

5. The potential difference between two points in a circuit is measured as 9.0 V. If the current flowing through the circuit is 75 A, what is the resistance in the circuit?
Given: $V = 9.0 \text{ V}$, $I = 75 \text{ A}$ Find: $R = ?$

$$R = \frac{I}{V} = \frac{75\text{A}}{9.0\text{V}} = 8.3333\Omega = 8.3\Omega$$

(final answer has 2 sig fig)

6. The potential difference between two points in a circuit is measured as 6.0 V. If the current flowing through the circuit is 58 A, what is the resistance in the circuit?
Given: Find:

7. The potential difference between two points in a circuit is measured as 15.0 V and the resistance in the circuit is 2.3 Ω , what is the current flowing through the circuit?
Given: Find:

8. The current flowing through the circuit is measured as 84 A. If the resistance in the circuit is 0.96 Ω , what is the potential difference between two points in the circuit?
Given: Find:

9. The current flowing through the circuit is measured as 150 A. If the resistance in the circuit is 4.22 Ω , what is the voltage in the circuit?
Given: Find: