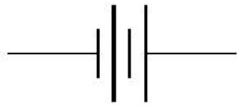











Parts of a Circuit

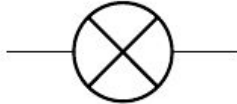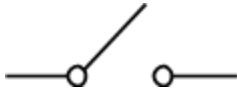Diagram	Name
	battery
	a single cell
	resistor
	lamp
	an open switch
	a closed switch
	ammeter
	voltmeter
	ohmmeter
	motor