

Calculate the total resistance, R_T , in each circuit:

